

CSE271 Section 2

Introduction to Digital Systems

Lecture 30

Instructor: Lin Li
<http://www.cse.psu.edu/~lili/cse271>

Derivation of State Table/Diagram

- Recall the first three steps of sequential system design:
 - ❖ Determine what needs to be stored in memory -- what are the possible states?
 - ❖ Code the inputs and outputs in binary.
 - ❖ Derive a state table or state diagram.
- Now, we start with verbal description of sequential system and develop state table/diagram.

Example 1

- A system with one input x and one output z , such that $z=1$ iff x has been 1 for at least three consecutive clock times.

Solution 1: store the last three inputs. Knowing them we could determine the output.

$q_1 q_2 q_3$	$q_1^* q_2^* q_3^*$		z
	$x = 0$	$x = 1$	
0 0 0	0 0 0	0 0 1	0
0 0 1	0 1 0	0 1 1	0
0 1 0	1 0 0	1 0 1	0
0 1 1	1 1 0	1 1 1	0
1 0 0	0 0 0	0 0 1	0
1 0 1	0 1 0	0 1 1	0
1 1 0	1 0 0	1 0 1	0
1 1 1	1 1 0	1 1 1	1

We store the oldest input in q_1 , and most recent one in q_3 .

When updating memory, we discard the oldest input stored.

8 states are required and 3 flip flops are needed.

$$q_3^* = x$$

$$q_2^* = q_3$$

$$q_1^* = q_2$$

3

Example 1

- A system with one input x and one output z , such that $z=1$ iff x has been 1 for at least three consecutive clock times.

Solution 2: store the number of consecutive 1's in memory.

A: none -- the last input was 0.

B: one

C: two

D: three or more

q	q^*		z
	$x = 0$	$x = 1$	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

4 states are required and 2 flip flops are needed.

4

Example 2

- A system with one input x and one output z , such that $z=1$ iff x is currently 1 and was also 1 at the previous two clock times.

Timing trace for CE6:

It's a Moore model.

x	0	1	1	0	1	1	1	0	0	1	0	1	1	1	1	0	0
z	?	0	0	0	0	0	0	1	0	0	0	0	0	0	1	1	1

Timing trace for CE7:

It's a Mealey model.

x	0	1	1	0	1	1	1	0	0	1	0	1	1	1	1	1	0
z	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	1	1

5

Example 2

- A system with one input x and one output z , such that $z=1$ iff x is currently 1 and was also 1 at the previous two clock times.

Solution 1: store the last two inputs.

q_1q_2	$q_1^*q_2^*$		z	
	$x=0$	$x=1$	$x=0$	$x=1$
00	00	01	0	0
01	10	11	0	0
10	00	01	0	0
11	10	11	0	1

6

Example 2

- A system with one input x and one output z , such that $z=1$ iff x is currently 1 and was also 1 at the previous two clock times.


Solution 2: store the number of consecutive 1's in memory.

A: none -- the last input was 0.

B: one

C: two

q	q*		z	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	A	C	0	1

 

7

Example 3

- Design both a Moore and a Mealy system with one input x and one output z , such that $z=1$ iff x has been 1 for *exactly* three consecutive clock times.

Sample timing trace:

x	0	1	1	1	1	1	0	1	1	0	1	1	1	0	1
z-Mealy	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
z-Moore	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0

We cannot tell whether there should be a 1 output when the third consecutive 1 input occurs.

We have to wait the next input arrives.


8

Example 3

- Design both a Moore and a Mealy system with one input x and one output z , such that $z=1$ iff x has been 1 for **exactly** three consecutive clock times.

Solution for Mealy system:

 A: no 1 in a row
 B: one 1 in a row
 C: two 1's in a row
 D: three 1's in a row
 E: more than three 1's in a row



9

Example 3

- Design both a Moore and a Mealy system with one input x and one output z , such that $z=1$ iff x has been 1 for **exactly** three consecutive clock times.

Solution for Moore system:

A: no 1 in a row
 B: one 1 in a row
 C: two 1's in a row
 D: three 1's in a row
 E: more than three 1's in a row
 F: three 1's plus a 0

q	q*		z
	x = 0	x = 1	
A	A	B	0
B	A	C	0
C	A	D	0
D	F	E	0
E	A	E	0
F	A	B	1

10

Example 4

- Design a Mealy system where the inputs are considered in blocks of three. The output is 1 iff the input is 1 for all three inputs in a block.

Sample timing trace:


x	0	1	1	1	1	1	1	0	1	1	1	0	1	1	1
z	0	0	0	0	0	1	0	0	0	0	0	0	0	0	1

11


Example 4

- Design a Mealy system where the inputs are considered in blocks of three. The output is 1 iff the input is 1 for all three inputs in a block.

Solution 1:

 

Solution 2:

 

12

Example 5

- Design a Moore system whose output is 1 iff three consecutive 0 inputs occurred more recently than three consecutive 1 inputs.

Sample timing trace:

x	1	1	1	0	0	1	0	1	1	1	0
z	?	?	?	0	0	0	0	0	0	0	0

x	0	1	0	0	0	0	1	1	1	1	0
z	0	0	0	0	0	0	1	1	1	1	0

