

CSE271 Section 2


Introduction to Digital Systems

Lecture 31

Instructor: Lin Li
<http://www.cse.psu.edu/~lili/cse271>

Shift Registers

 - A register is a collection of flip flops, with a common name and a common clock.
- Shift register -- data moves one place to the right on each clock or shift input.




Red NOT gate

- ❖ Leading-edge triggered shift register
- ❖ Circuit presents a load of 1 to the clock, rather than a load of 4.

Serial-in Serial-out Shift Register

 
Only 1 bit (at left) may be loaded into the register at a time and only 1 bit (at right) may be read.



x	1	0	1	1	1	0	1	1	1	1	0	0	0
q ₁	0	1	0	1	1	1	0	1	1	1	1	0	0
q ₂	0	0	1	0	1	1	1	0	1	1	1	1	0
q ₃	0	0	0	1	0	1	1	1	0	1	1	1	1
q ₄	0	0	0	0	1	0	1	1	1	0	1	1	1

3

Application: Shift Register Storage

 

When load=0, the data circulate around the n flip flops.


Data is available only at q_n, once every n clock cycles.

When load=1, x can be stored into q₁.

To initialize register to all 0's, we can let x=0 and load=1 for n clock cycles.

4

Serial-in Parallel-out Shift Register

 

D flip flop implementation.

We can initialize the register using $clear'$ input.

Application: input port from modem
(converting serial data to parallel data).

5


Parallel-in Serial-out Shift Register

If $load'=0$, $IN_2=0$, then $PRE'=1$ and $CLR'=0$, $q_2=0$. (static loading)

$IN_2=1$, then $PRE'=0$ and $CLR'=1$, $q_2=1$.

If $load'=1$, $Enable'=0$, then clock is inverted and goes through. Register shifts.


$Enable'=1$, Register does not shift.

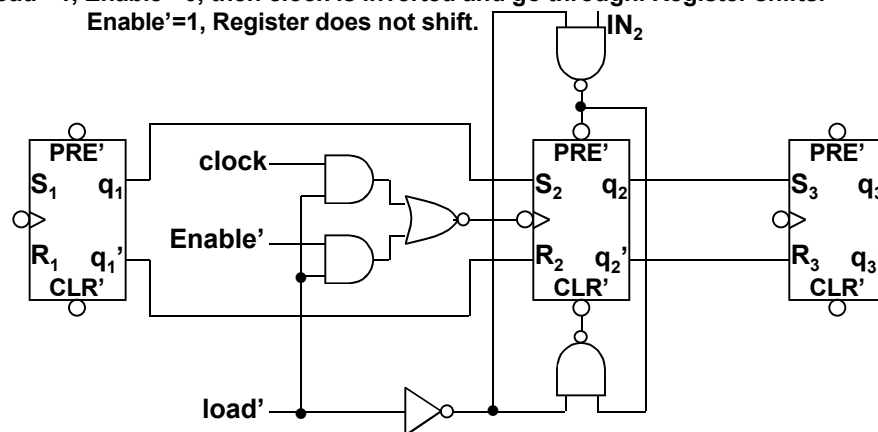

6


Parallel-in Serial-out Shift Register

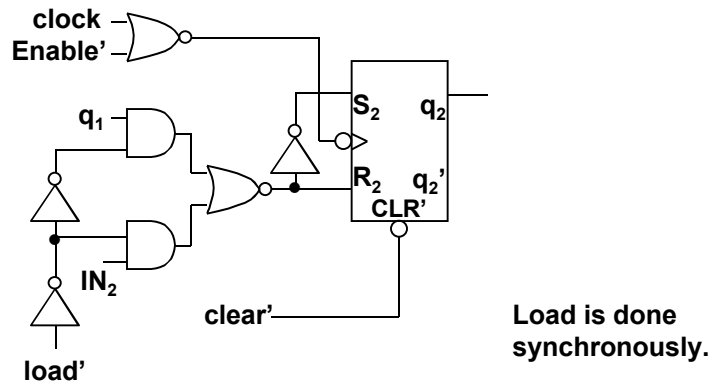There is an independent active low static clear.
 When Enable'=0, clock is inverted and go through.
 When Enable'=0 and load'=0, IN_2 is stored into q_2 .
 When Enable'=0 and load'=1, q_1 is shift into q_2 .



7

Right/Left Shift Register

 

Most computers include both left/right shift and rotate instructions. Right/left shift register can shift the stored bits in both directions.

	Clear'	S ₀	S ₁	q ₁ *	q ₂ *	q ₃ *	q ₄ *
Static clear	0	X	X	0	0	0	0
Hold	1	0	0	q ₁	q ₂	q ₃	q ₄
Shift left	1	0	1	q ₂	q ₃	q ₄	LS
Shift right	1	1	0	RS	q ₁	q ₂	q ₃
Load	1	1	1	IN ₁	IN ₂	IN ₃	IN ₄

8

Application of Right/Left Shift Register

- Typically used in ALU for better performance
 - ❖ Multiplied by 2 can be done by one-bit shifting left.
 - 4×2 : 0100 shift left one bit and get 1000 (8).
 - ❖ Divided by 2 can be done by one-bit shifting right.
 - $4/2$: 0100 shift right one bit and get 0010 (2).