

# LOGIC DESIGN OF SEQUENTIAL CIRCUITS

---


- ❁ **General Model of Sequential Circuit**
- ❁ **Flip-Flop as Basic Memory Unit**
- ❁ **Analysis of Sequential Circuits**
- ❁ **Design of Sequential Circuits**
- ❁ **Sequential MSI Modules**

## *General Model of Sequential Circuit*

---

- ❁ Output depends on circuit's history stored as state variables in memory.
- ❁ Mealy machine:  $\text{outputs} = F(\text{inputs}, \text{current states})$
- ❁ Moore machine:  $\text{outputs} = F(\text{current states})$   
It has no input variables other than the clock.
- ❁ Excitation signals act on memory for next states.

# *General Model of Sequential Circuit*

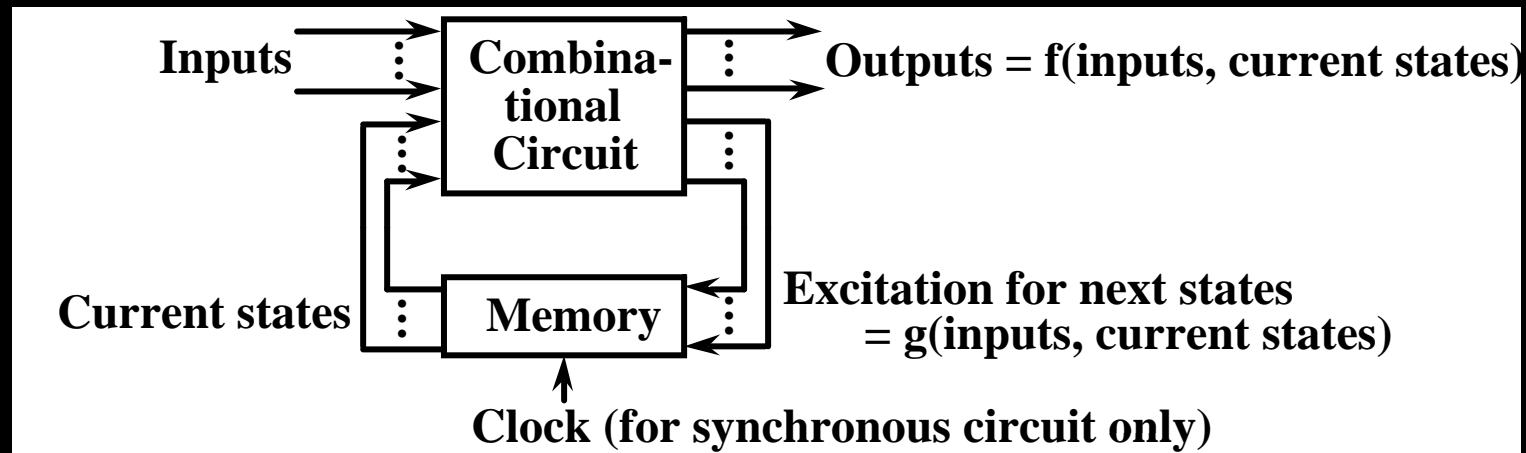

- ❁ Synchronous circuit — State changes only at the occurrence of clock.
- ❁ Asynchronous circuit — State changes in response to the change of inputs.

# *FLIP-FLOP AS BASIC MEMORY UNIT*

## A Simple SR Latch

---

A simple SR Latch with two stable states:

$Q=0$ ,       $Q'=1$       in '0' state;


$Q=1$ ,       $Q'=0$       in '1' state.

$S(\text{set})$ ,       $R(\text{reset})$  — excitation signals.

# FLIP-FLOP AS BASIC MEMORY UNIT



 
## A Simple SR Latch

❁ Conceptual circuit: symbol, state transition table & analysis



S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	not defined
1	1	1	not defined

} Q(t+1)=Q(t)  
} Q(t+1)=0  
} Q(t+1)=1

  
 


# FLIP-FLOP AS BASIC MEMORY UNIT (continued)
  
## Clocked SR flip-flop

⊗ Flip-flop changes state only when clock = 1.

Conceptual ckt, symbol, state transition table & equation:




S	R	Q(t)	Q(t+1)	
0	0	0	0	} Q(t+1)=Q(t)
0	0	1	1	
0	1	0	0	} Q(t+1)=0
0	1	1	0	
1	0	0	1	} Q(t+1)=1
1	0	1	1	
1	1	0	not defined	
1	1	1	not defined	

$$Q(t+1) = S + R'Q(t)$$

SR = 0 (restriction)

 ⊗ State transition diagram & excitation table:





Q(t)	Q(t+1)	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

# FLIP-FLOP AS BASIC MEMORY UNIT (continued)
  
## Clocked JK flip-flop

❁ Extension of SR FF by allowing  $J=1$  &  $K=1$ .


Conceptual ckt, symbol, state transition table & equation:



J	K	Q(t)	Q(t+1)	
0	0	0	0	} Q(t+1)=Q(t)
0	0	1	1	
1	0	0	0	} Q(t+1)=0
1	0	1	0	
0	1	0	1	} Q(t+1)=1
1	1	1	1	
		0	1	} Q(t+1)=Q(t)'
		1	0	

$$Q(t+1) = JQ(t)' + K'Q(t)$$

 ❁ State transition diagram & excitation table:





Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

# FLIP-FLOP AS BASIC MEMORY UNIT (continued)
  
## Clocked T flip-flop


- ❖ A special case of JK FF by setting  $J=K=T$ .  
Conceptual ckt, symbol, state transition table & equation:



T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

$$Q(t+1) = TQ(t)' + T'Q(t) = T \oplus Q(t)$$

 - ❖ State transition diagram & excitation table:



Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0





# FLIP-FLOP AS BASIC MEMORY UNIT (continued)
  
## Clocked D flip-flop

❁ A special case of JK FF by setting  $J=\bar{K}=D$ .


Conceptual ckt, symbol, state transition table & equation:



D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

$$Q(t+1) = D$$

 ❁ State transition diagram & excitation table:



Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

# FLIP-FLOP AS BASIC MEMORY UNIT (continued)


## Edge-triggered flip-flop

⊗ FF changes state only at the edge of the clock.

solves the problem of multiple triggering of level-controlled FF when level is active. Two methods of circuit implementation:

- ◇ master-slave flip-flop
- ◇ special circuit

 Typical waveforms of edge-triggered JK FF:



⊗ In the setup time, J,K must be constant prior to the active edge of the clock.

⊗ In the hold time, J,K must not change after the active edge of the clock.

# ANALYSIS OF SEQUENTIAL CIRCUITS


Write logical expressions for excitation and output in terms of input and current state. Write state transition table and output table. Draw the state transition diagram.

## Example 4.1

$$J_1 = x \oplus A_0' \quad K_1 = 1$$

$$J_0 = A_1 \quad K_0 = 1$$

$$F = A_1$$

 

x	Current						Next State		F
	A <sub>1</sub>	A <sub>0</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>	A <sub>1(t+1)</sub>	A <sub>0(t+1)</sub>	
0	0	0	1	1	0	1	1	0	0
0	0	1	0	1	0	1	0	0	0
0	1	0	1	1	1	1	0	1	1
0	1	1	0	1	1	1	0	0	1
1	0	0	0	1	0	1	0	0	0
1	0	1	1	1	0	1	1	0	0
1	1	0	0	1	1	1	0	1	1
1	1	1	1	1	1	1	0	0	1


When x=0,  
00->10->01->00->...

When x=1,  
01->10->01->...

Self-correcting:

x=0, 11->00

x=1, 11->00, 00->00

 

# DESIGN OF SEQUENTIAL CIRCUITS

## Design of a Gray Code Counter (Example 4.2)

---

### ⊗ Problem specification.

For the counter,

- find state transition table.
- Excitation table for the type of chosen FF.
- Simplest expressions of excitation signals.
- Check the self-correcting property. If not correct, modify the design.
- Implement the counter, then the system.

### ⊗ Example

Design a counter for the given Gray code subsequence:

000 → 001 → 011 → 010 → 110 → 100 → 000 (repeat)

# DESIGN OF SEQUENTIAL CIRCUITS (continued)

## Design of the counter using JK FF's

Counting sequence      state transition table  
State transition table      Excitation table

current			next			Excitation for JK FF's					
$y_2$	$y_1$	$y_0$	$y_2^+$	$y_1^+$	$y_0^+$	$J_2$	$K_2$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	1	0	x	1	x	x	0
0	1	0	1	1	0	1	x	x	0	0	x
0	1	1	0	1	0	0	x	x	0	x	1
1	0	0	0	0	0	x	1	0	x	0	x
1	0	1	x	x	x	x	x	x	x	x	x
1	1	0	1	0	0	x	0	x	1	0	x
1	1	1	x	x	x	x	x	x	x	x	x

$y_2 \backslash y_1$	00	01	11	10
0	0	1	x	x
1	0	0	x	x

$J_2 = y_1 \bar{y}_0$

$y_2 \backslash y_1$	00	01	11	10
0	x	x	0	1
1	x	x	x	x

$K_2 = \bar{y}_1$

$y_2 \backslash y_1$	00	01	11	10
0	0	x	x	0
1	1	x	x	x

$J_1 = y_0$

$y_2 \backslash y_1$	00	01	11	10
0	x	0	1	x
1	x	0	x	x


$K_1 = y_2$

$y_2 \backslash y_1$	00	01	11	10
0	1	0	0	0
1	x	x	x	x

$J_0 = \bar{y}_2 \bar{y}_1$

$y_2 \backslash y_1$	00	01	11	10
0	x	x	x	x
1	0	1	x	x

$K_0 = y_1$

 

⊛ Self-correcting:  
101 -> 011  
111 -> 100

# DESIGN OF SEQUENTIAL CIRCUITS (continued)

## Design of the counter using D FF's

### State transition table & Excitation table

current			next			Excitation		
$y_2$	$y_1$	$y_0$	$y_2^+$	$y_1^+$	$y_0^+$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	1
0	1	0	1	1	0	1	1	0
0	1	1	0	1	0	0	1	0
1	0	0	0	0	0	0	0	0
1	0	1	x	x	x	x	x	x
1	1	0	1	0	0	1	0	0
1	1	1	x	x	x	x	x	x

		$y_2 y_1$			
$y_0$		00	01	11	10
	0	0	1	1	0
	1	0	0	x	x


$D_2 = y_1 \bar{y}_0$

		$y_2 y_1$			
$y_0$		00	01	11	10
	0	0	1	0	0
	1	1	1	x	x

$D_1 = \bar{y}_2 y_1 + y_0$

		$y_2 y_1$			
$y_0$		00	01	11	10
	0	1	0	0	0
	1	1	0	x	x

$D_0 = \bar{y}_2 \bar{y}_1$

 


⊗ Self-correcting:  
 101 → 010  
 111 → 010


# SEQUENTIAL MSI MODULES

## Shift Register & Shift Operations

- ❁ Left shift, e.g., on JK FF's

 


- ❁ Logical right shift, e.g., on D FF's

 

- ❁ Arithmetic right shift: connect MSB to shift in  
Arithmetic left shift: signal overflow if the sign changes.
- ❁ Rotate: connect shift in & shift out

# SEQUENTIAL MSI MODULES (continued)

## Bidirectional Shift Register

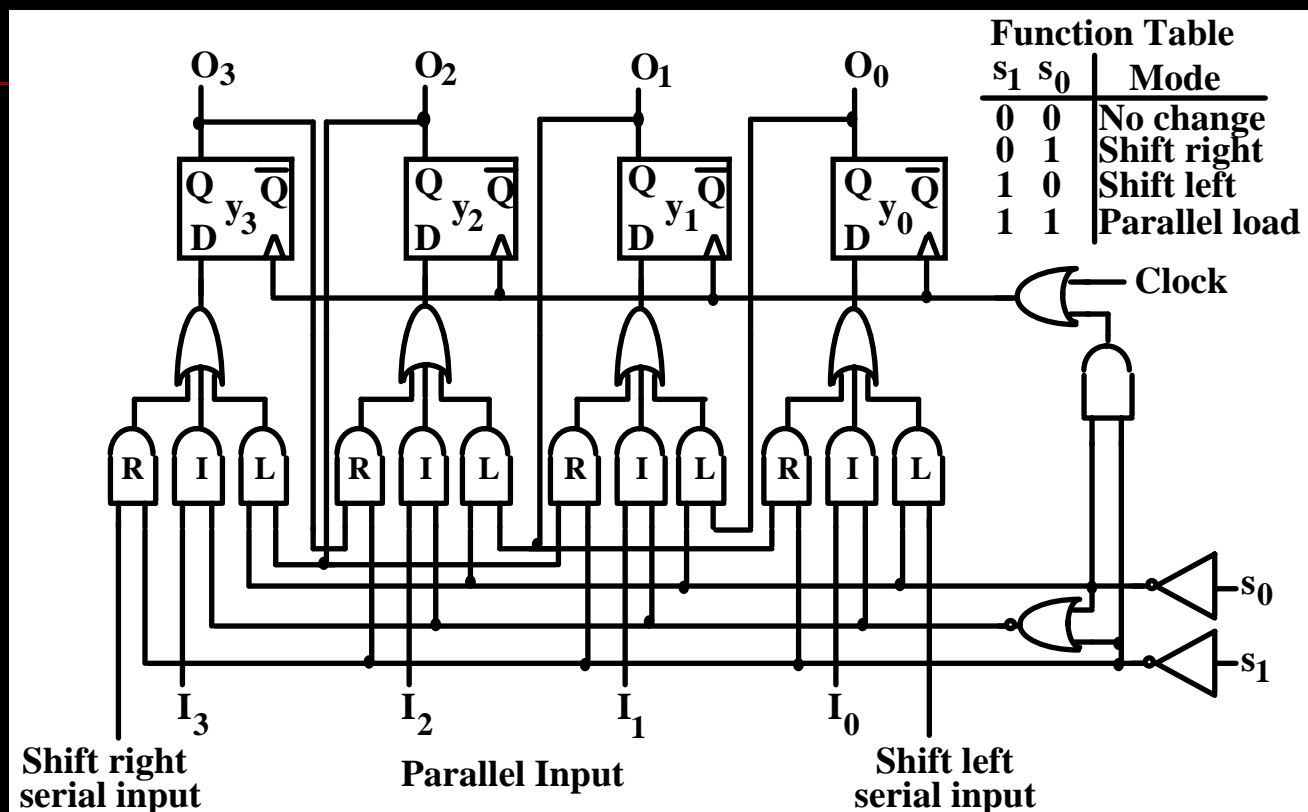

To maintain D FF unaltered, either feedback Q to D or block the clock.



# SEQUENTIAL MSI MODULES (continued)

## Ripple-Carry Binary Counter


current $y_2 y_1 y_0$	Count up next $y_2^+ y_1^+ y_0^+$			Count down next $y_2^+ y_1^+ y_0^+$		
	$y_2^+$	$y_1^+$	$y_0^+$	$y_2^+$	$y_1^+$	$y_0^+$
0 0 0	0	0	1	1	1	1
0 0 1	0	1	0	0	0	0
0 1 0	0	1	1	0	0	1
0 1 1	1	0	0	0	1	0
1 0 0	1	0	1	0	1	1
1 0 1	1	1	0	1	0	0
1 1 0	1	1	1	1	0	1
1 1 1	0	0	0	1	1	0

### Count up

$y_0$  triggers every clock.  
 $y_1$  triggers if  $y_0=1$ .  
 $y_2$  triggers if  $y_1 y_0=1$ .  
 $y_i$  triggers if  $y_{i-1} \dots y_0=1$ .
 
### Count down


$y_0$  triggers every clock.  
 $y_1$  triggers if  $y_0=1$ .  
 $y_2$  triggers if  $y_1 y_0=1$ .  
 $y_i$  triggers if  $y_{i-1} \dots y_0=1$ .




## SEQUENTIAL MSI MODULES (continued)

## Counter on D FF's & Parallel Counter

# Parallel Counter

 


## Counter on D FF's

 

# SEQUENTIAL MSI MODULES (continued)

## Up/Down Counter

Up/Down Counter selected by XOR gates

 

## Multifunctional Up/Down Counter

Function Table

$s_1$	$s_0$	Mode
0	0	Clear
0	1	No action
1	0	Count up
1	1	Count down

