

CSE271 Section 2

Introduction to Digital Systems

Lecture 29

Instructor: Lin Li
<http://www.cse.psu.edu/~lili/cse271>

Synchronous Counter

- Basic format of synchronous counters
 - ❖ No data input
 - ❖ Go through a fixed sequence of states on successive clocks
 - ❖ The output is the state of the system
- Example: a counter with the following sequence:
0,1,2,3,4,5,6,7,8,9,10,11,12,13,14,15,0,1,2,.....
 - ❖ 16 states -- require coding with 4-bit binary
 - ❖ 4-bit binary counter

Synchronous Counter (Cont'd)

| D | C | B | A | D* | C* | B* | A* |
|---|---|---|---|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | 1 | 1 |
| 01 | | | 1 | 1 |
| 11 | | 1 | | 1 |
| 10 | | | 1 | 1 |

D*

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | 1 | 1 | |
| 01 | | 1 | 1 | |
| 11 | 1 | | | 1 |
| 10 | | 1 | 1 | |

C*

$$\begin{aligned}
 D_D = D^* &= DC' + DB' + DA' + D'CBA \\
 &= D(C' + B' + A') + D'CBA \\
 &= D(CBA)' + D'CBA \\
 &= D \oplus (CBA) \\
 D_C = C^* &= CB' + CA' + C'BA \\
 &= C \oplus (BA)
 \end{aligned}$$

3

Synchronous Counter (Cont'd)

| D | C | B | A | D* | C* | B* | A* |
|---|---|---|---|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | | |
| 01 | 1 | 1 | 1 | 1 |
| 11 | | | | |
| 10 | 1 | 1 | 1 | 1 |

B*


| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | 1 | 1 | 1 |
| 01 | | | | |
| 11 | | | | |
| 10 | 1 | 1 | 1 | 1 |

A*

$$\begin{aligned}
 D_B = B^* &= B'A + BA' \\
 &= B \oplus A \\
 D_A = A^* &= A'
 \end{aligned}$$

4

Synchronous Counter (Cont'd)

 

$$\begin{aligned} J_D &= K_D = CBA \\ J_C &= K_C = BA \\ J_B &= K_B = A \\ J_A &= K_A = 1 \end{aligned}$$

The blue AND gate is not necessary.
 OV is 1 when the counter is in state 15 (1111).
 Extend the design to 5 or more flip flops:
 $J_E = K_E = DCBA$
 $J_F = K_F = EDCBA \dots\dots$

7

Up/down Counter

| x | C | B | A | C* | B* | A* |
|---|---|---|---|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 |

A counter that can count in either direction, depending upon a control input, labeled as x.

When x=0, the counter has following sequence: 0,1,2,3,4,5,6,7,0,1.....

When x=1, the counter has following sequence: 7,6,5,4,3,2,1,0,7,6,.....

8

Up/down Counter (Cont'd)

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | 1 | | 1 |
| 01 | | 1 | 1 | |
| 11 | 1 | | 1 | |
| 10 | | 1 | 1 | |

C^*

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | 1 | 1 |
| 01 | 1 | 1 | | |
| 11 | | | 1 | 1 |
| 10 | 1 | 1 | | |

B^*

| DC \ BA | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | 1 | 1 | 1 |
| 01 | | | | |
| 11 | | | | |
| 10 | 1 | 1 | 1 | 1 |

A^*


$$J_C = K_C = x'BA + xB'A'$$

$$J_B = K_B = x'A + xA'$$

$$J_A = K_A = 1$$

9

Up/down Counter (Cont'd)

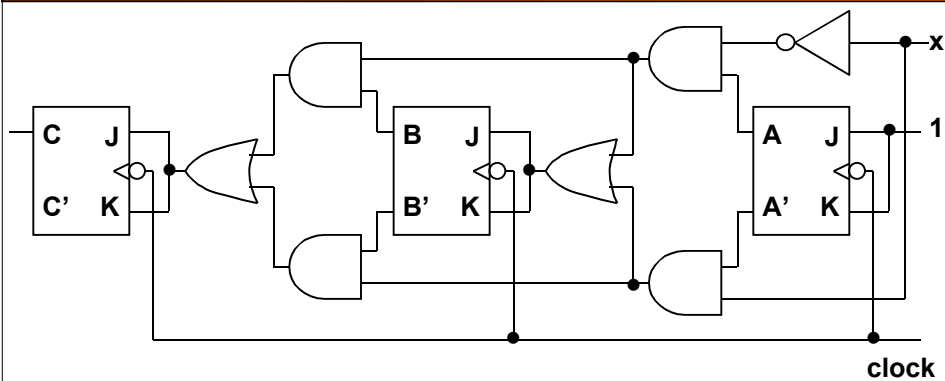

$$J_C = K_C = x'BA + xB'A'$$

$$J_B = K_B = x'A + xA'$$

$$J_A = K_A = 1$$

Extend the design to 4 or more flip flops:

$$J_D = K_D = x'CBA + xC'B'A'$$

$$J_E = K_E = x'DCBA + xD'C'B'A' \dots\dots$$

10

Decimal Counter

| D | C | B | A | D* | C* | B* | A* |
|---|---|---|---|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | X | X | X | X |
| 1 | 0 | 1 | 1 | X | X | X | X |
| 1 | 1 | 0 | 0 | X | X | X | X |
| 1 | 1 | 0 | 1 | X | X | X | X |
| 1 | 1 | 1 | 0 | X | X | X | X |
| 1 | 1 | 1 | 1 | X | X | X | X |

A counter that goes through the sequence:
0,1,2,3,4,5,6,7,8,9,0,1.....

11

Decimal Counter (Cont'd)

| DC | BA | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | | | | X | 1 |
| 01 | | | | X | |
| 11 | | | 1 | X | X |
| 10 | | | | X | X |

D*

| DC | BA | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | | | | X | |
| 01 | | 1 | 1 | X | |
| 11 | | | | X | X |
| 10 | | 1 | 1 | X | X |

B*

| DC | BA | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | | | 1 | X | |
| 01 | | | 1 | X | |
| 11 | | 1 | | X | X |
| 10 | | | 1 | X | X |

C*

| DC | BA | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| 00 | | 1 | 1 | X | 1 |
| 01 | | | | X | |
| 11 | | | | X | X |
| 10 | | 1 | 1 | X | X |

A*

$$\begin{aligned}
 J_D &= CBA \\
 K_D &= A \\
 J_C &= K_C = BA \\
 J_B &= D'A \\
 K_B &= A \\
 J_A &= K_A = 1
 \end{aligned}$$

12

Initial State of Counters

- We do not know in what state each flip flop will be initially, when we turn the system on.
 - ❖ Often, all we care about is that once the system is turned on, it goes through the desired sequence after one or two clocks.
 - ❖ If we care about the initial state,
 - Use some combination of clears and presets to get the system into the proper initial state.

13

Counter with Unused States


A counter that goes through the following sequence that is not in numeric order: 0,3,2,4,1,5,7, and repeat.

| C | B | A | C* | B* | A* |
|---|---|---|----|----|----|
| 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | X | X | X |
| 1 | 1 | 1 | 0 | 0 | 0 |

$$D_C = BA' + B'A$$

$$D_B = C'B'A' + C'BA + CB'A$$

$$D_A = B'$$

 

If CBA=110, $D_C D_B D_A = 100$.
 After the design, there are no any don't cares.
 With different designs, the next state of the state "110" is different.

14

Cycling/Saturating Counter

A 2-bit up/down, cycling/saturating counter with two control inputs x and y:

If $x=0$, it counts up;

If $x=1$, it counts down;

If $y=0$, it cycles -- 0,1,2,3,0,1,..... or 3,2,1,0,3,2,.....

If $y=1$, it saturates -- 0,1,2,3,3,3,..... or 3,2,1,0,0,0,.....

| AB | A*B* | | | |
|----|---------|---------|---------|---------|
| | xy = 00 | xy = 01 | xy = 10 | xy = 11 |
| 00 | 01 | 01 | 11 | 00 |
| 01 | 10 | 10 | 00 | 00 |
| 10 | 11 | 11 | 01 | 01 |
| 11 | 00 | 11 | 10 | 10 |


15

Asynchronous Counter

➤ Asynchronous counter

- ❖ Counters without a clock input.
- ❖ Each flip flop is triggered by the transition of the previous one.
- ❖ Advantage -- the simplicity of the hardware.
- ❖ Disadvantage -- longer delay.
 - ▢ Flip flop B changes later than flip flop A.


➤ Count signal may be irregular.

 

go through the sequence 00,01,10,11, and repeat.

16


4-bit Asynchronous Counter

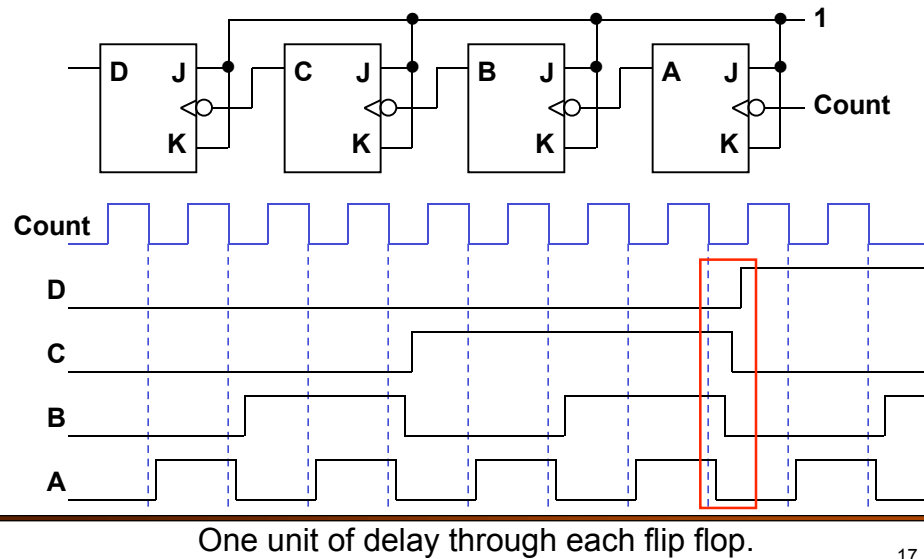

17

Asynchronous Counter with Reset

 Design an asynchronous base-12 counter with sequence 0,1,2,3,4,5,6,7,8,9,10,11,0,1,.....



Use a 4-bit binary counter and reset it when it reaches 12. Note that it remains in state 12 for a short time, due to the delay of flip flops.

18